## 2023 Digital IC Design Homework 1

NAME		何坤	霖										
Student ID		N26112445											
Functional Simulation Result													
Stage 1	P	ass	Stage 2	Pass	Stage 3	Pass	Stage 4	Pass					
Stage 1													
ModelSim> run -all #Stage 1 : Maximum selection with 4-input MMS # #Stage 1 : Pass!													
Stage 2													
#Stage 2 : Minimum selection with 4-input MMS #Stage 2 : Pass!													
				Stag	ge 3								
# #		-Stage -Stage		m selection Pas:	n with 8-in	nput MMS							
Stage 4													
# # # #		-Stage -Stage		m selection Pas:	n with 8-in	put MMS							
# Simulation finish, ALL PASS													
Description of your design													

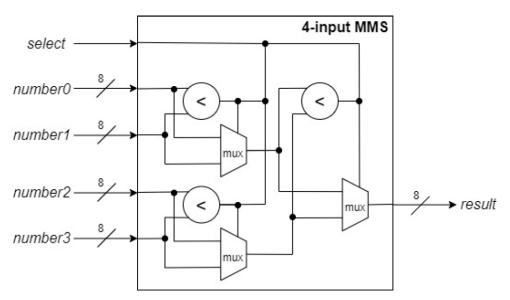


Fig. 1. The logic diagram of the 4-input MMS.

依照上圖要求區分出兩個 module (cmp 以及 muxMM)

cmp: 進行兩個輸入的大小判斷,再依據 multiplexer selection cases

當上面的輸入 $(num_a)$ 小於下面的輸入 $(num_b)$ 就設定成 1,反之為 0。

muxMM:使用 case 去實做判斷 sel\_cmp 對應就是下面的 table

Table II. The selection case of the multiplexer.

{select, cmp}	output
00	input1
01	input2
10	input2
11	Input1

select 為 1 表示要選擇最小的。

MMS\_4num: instantiate 設計出的 modules 把對應的線串接起來。 串線的關係可以根據命名看出,舉例 cmpS0\_0\_muxS0\_0,就是 stage0 的 cmp 的輸出到 stage0 的 muxMM,相同 module 的編碼由上而下,由 0

開始。

sim -gui -novopt work.	MMS tb		
vsim -gui -novopt wor	k.MMS tb		
Refreshing D:/Master	shit life/111-2/dic2023/HW	Ns/HWl/file/work.MMS_tb	
Loading work.MMS_tb		_	
Refreshing D:/Master	shit life/111-2/dic2023/HW	/s/HWl/file/work.MMS_4num	
Loading work.MMS_4num			
•	shit life/111-2/dic2023/HW	/s/HWl/file/work.cmp	
Loading work.cmp			
	shit life/111-2/dic2023/HW	/s/HWl/file/work.muxMM	
Loading work.muxMM			
•	shit life/111-2/dic2023/HW	s/HW1/file/work.MMS_8num	
Loading work.MMS_8num	1		
ModelSim> run -all	. Managaman and angel and a state of	i 10/5	
:Stage I	: Maximum selection with 4	-input MMS	
Stage 1	. Board		
Stage I	. rass:		
Stage 2	: Minimum selection with 4	-input MMS	
Stage 2	. Hilliam Scientin with	Input III	
Stage 2	: Pass!		
Stage 3	: Maximum selection with 8	-input MMS	
•			
Stage 3	: Pass!		
ŧ			
Stage 4	: Minimum selection with 8	-input MMS	
ŧ .			
Stage 4	: Pass!		
ŧ .			
	Ginnless Sinish 277 PT		
	Simulation finish, ALL PA	155	
tt Motor Cfinish	D./Magton shit life/111 3	?/dic2023/HWs/HW1/file/MMS tb.v(182	
	Iteration: 0 Instance: /M	The state of the s	-1